

Current Electricity

Continuous flow of electric charges



Did You Know?

The voltage across a muscle cell in your body is about 70 millivolts. A millivolt (mV) is one thousandth of a volt.

AC and DC

- DC
 - Direct Current
 - Electrons flow in one direction
 - e.g. battery
- AC
 - Alternating Current
 - Electrons flow changes direction
 - e.g. wall outlet (120Volts, 60 Hertz or vibrations per second)

In 1799, Volta invented a “voltaic pile” battery, alternating zinc and copper disks separated by pieces of fabric

soaked in salt water.




Alessandro Volta
(1745–1827)




Electric Potential Energy

Potential Difference

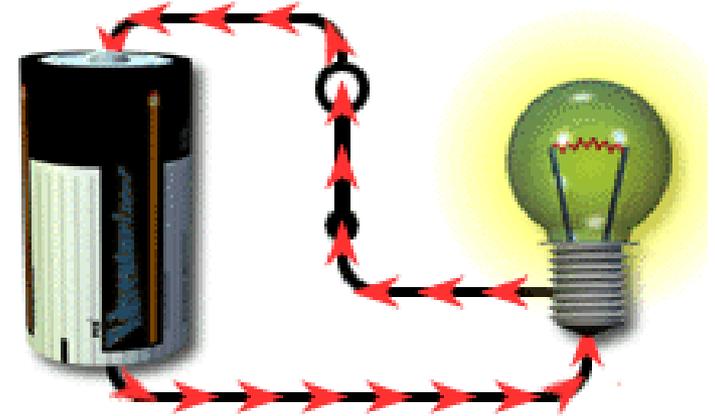


- stored energy from separating $+$ and $-$ charges or from pushing like charges together.
- Current will flow if:
 - 1) a difference in electrical potential energy can be maintained
 - 2) a complete pathway exists for charges to follow

A chemical cell

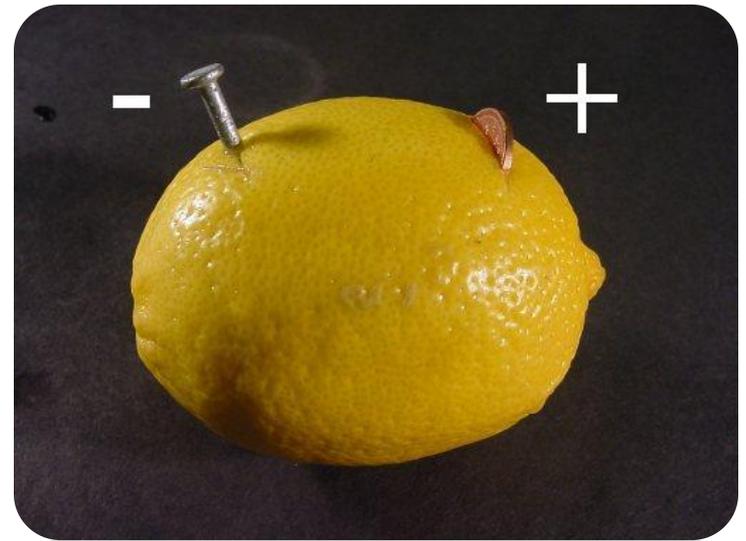

- 2 electrical connections (terminals) made of two different metals in a conducting solution
- chemical reactions create a source of electrons at one point and consume electrons at another
- “Dry Cells” - liquid conductor is replaced by a conducting paste (e.g. D - cell, AA - cell)

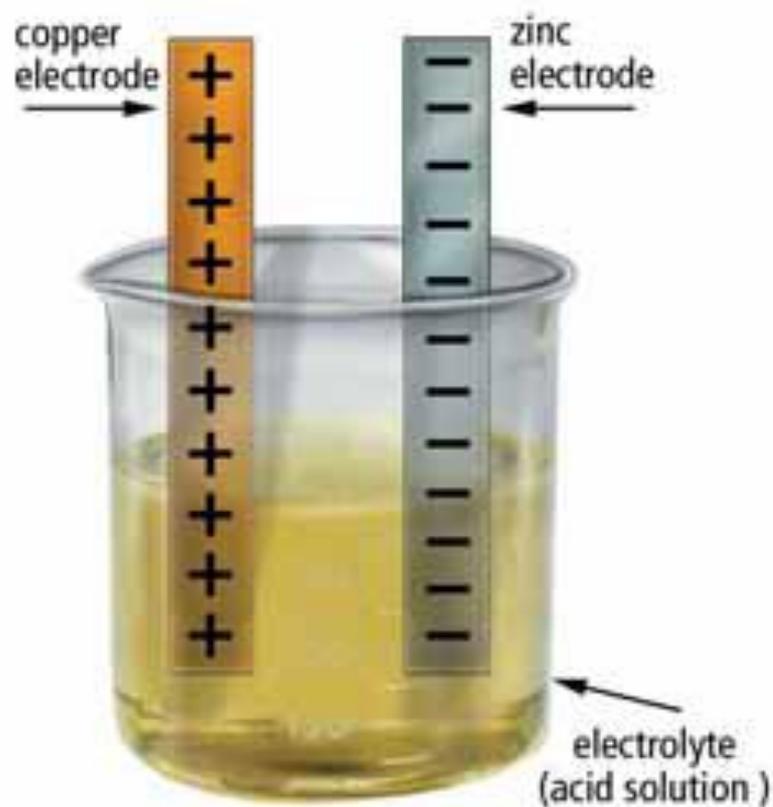An electrochemical cell requires two different electrodes (usually metals) and an electrolyte.




Different Types of Dry Cells



Battery

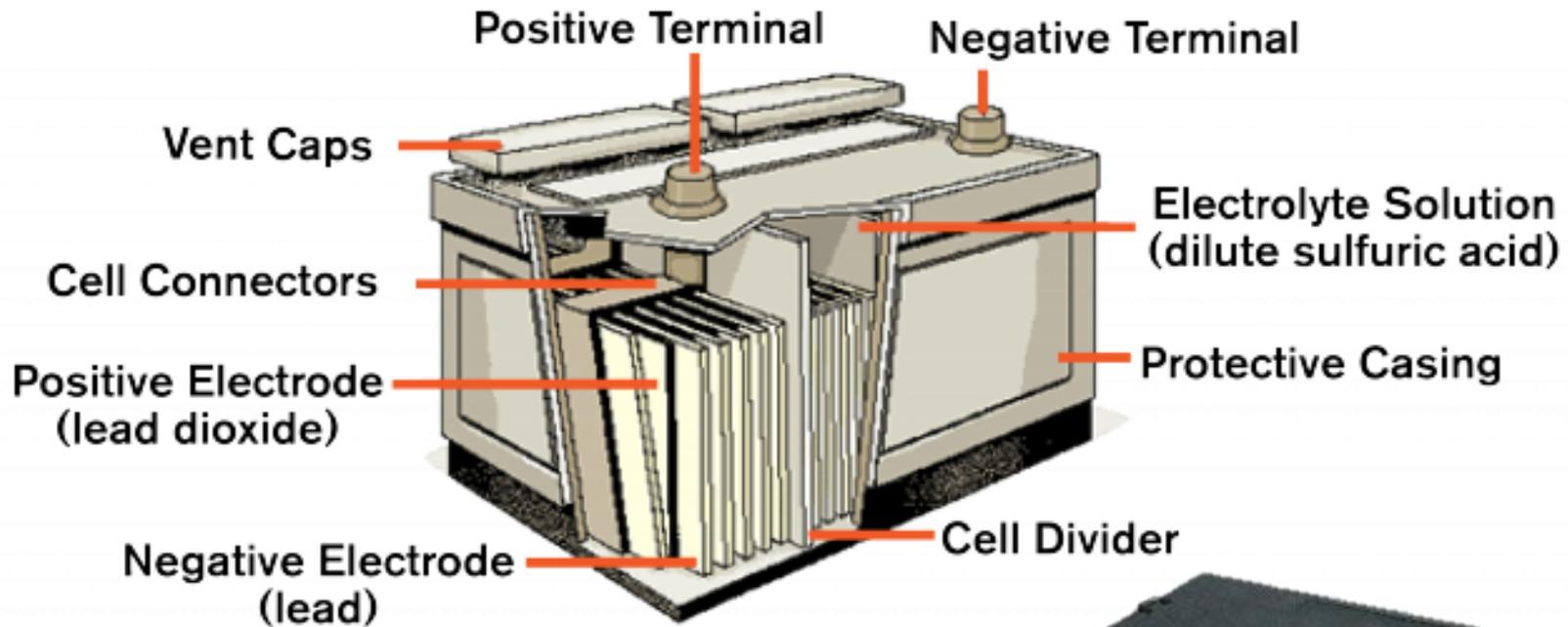- term is usually used incorrectly in everyday speech
- consists of 2 or more cells connected together
- e.g. car battery, group of AA or other cells connected together





Car Battery

What is a conductor?

- a material that allows free electron movement
- Examples:
 - Aluminum
 - Gold
 - Copper
 - Most Metals




Circuits

- A circuit is a closed path that electrons move through.


In circuits there are:

- Batteries as the energy source which provide the energy to push electric charges. This movement is called a current.
- A resistor represents loads which convert electrical energy to other forms like light, heat, motion and sound.
- Resistors all resist the movement of charge through the circuit.
- A switch is used to control the circuit.

CIRCUIT DIAGRAM

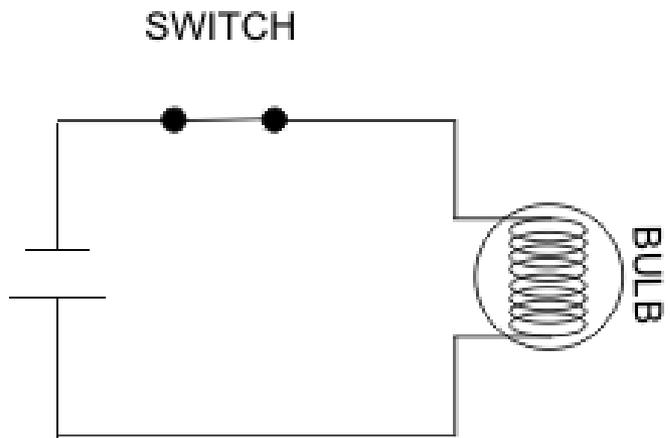

PICTORIAL CIRCUIT DIAGRAM

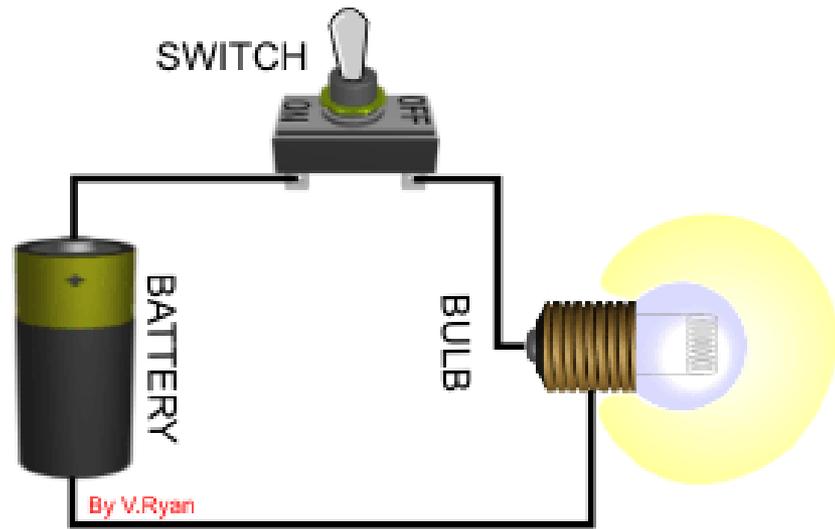

Units

- Electrical Charges are measured in Coulombs

1 coulomb of charge = 6.24×10^{18} charges

Voltage

- A measure of the electrical potential energy of the charges
- measured in Volts

$$1 \text{ Volt} = \frac{1 \text{ Joule of energy}}{1 \text{ Coulomb of charge}}$$

Current - a measure of the rate of flow of electrons

$$1 \text{ Ampere (or Amp)} = \frac{1 \text{ Coulomb of charge}}{\text{second}}$$



“Conventional Current”: flow of charges from + to -
(decided before it was known that electrons moved, not protons)

- Actual flow of charges (electrons) is from - to +


Continue lesson next day
Complete Booklet 8.1

ELECTRIC CIRCUITS

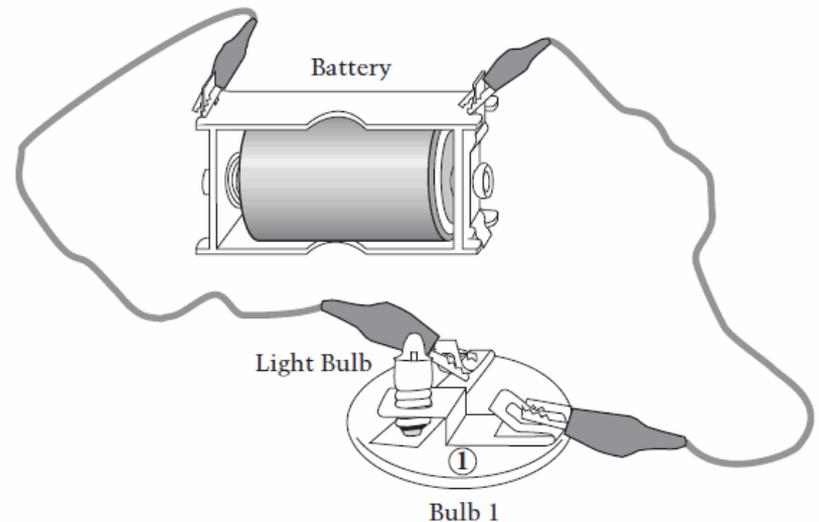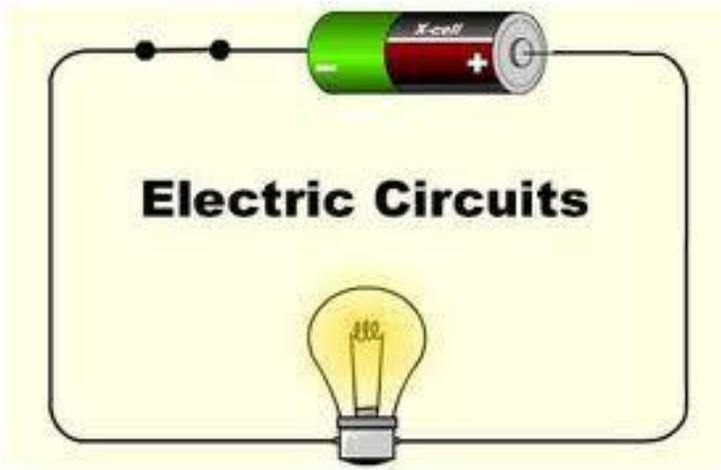- A complete conducting pathway for current from the source and back again
- Two different types of circuits depending on the number of pathways for the electrons



A Simple Circuit

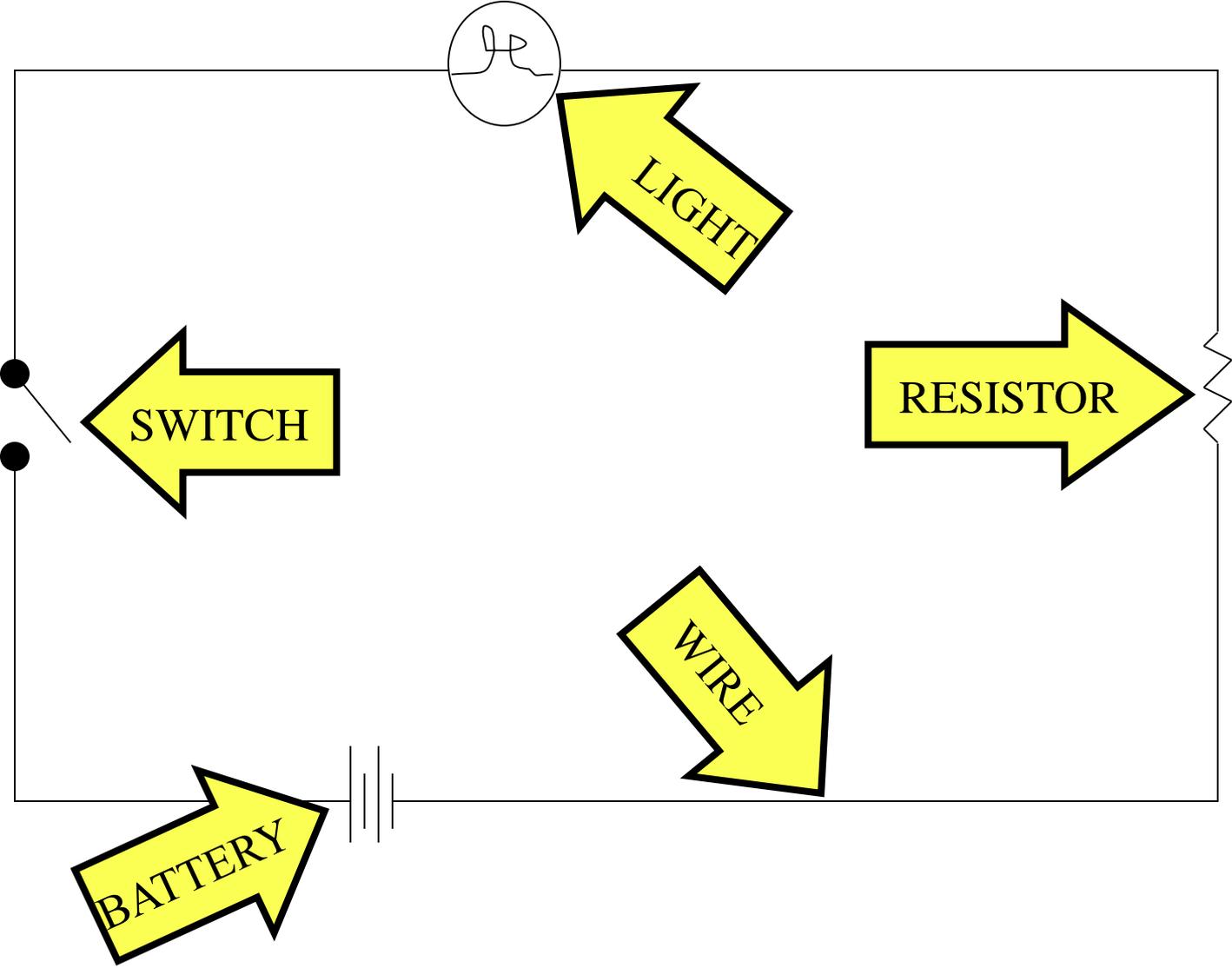

Load

There must be a device, called a load, which converts electrical energy into other forms of energy such as light or sound. Light bulbs, speakers, heaters, and motors are examples of loads.



Resistance

- a measure of how difficult it is for current to flow through a conductor
- measured in Ohms (Ω)


Resistor

- devices that “resist” flow of electricity
- turns electricity into heat and light (e.g. light bulb filament, heating element, toaster wires)





Rheostat

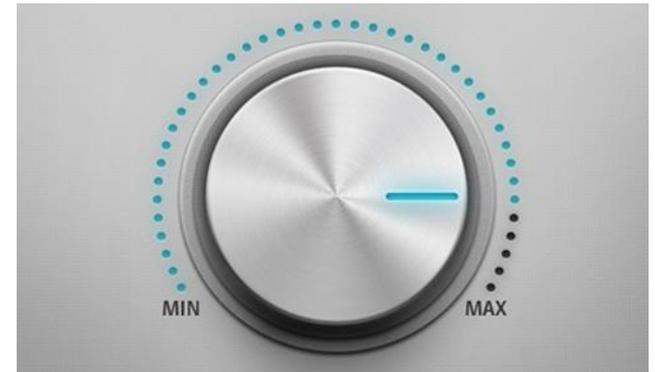- variable resistor
- Changes the amount of electricity that flows
- e.g. volume control, dimmer switch, temperature control





SERIES CIRCUIT

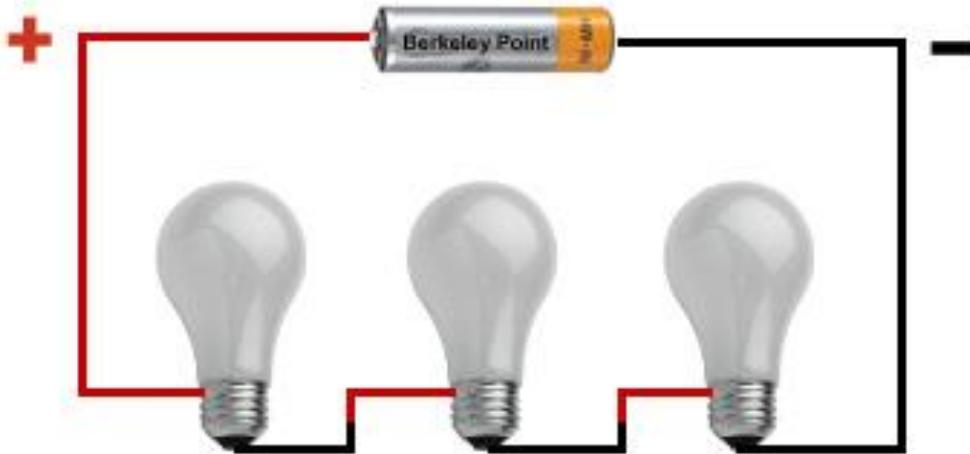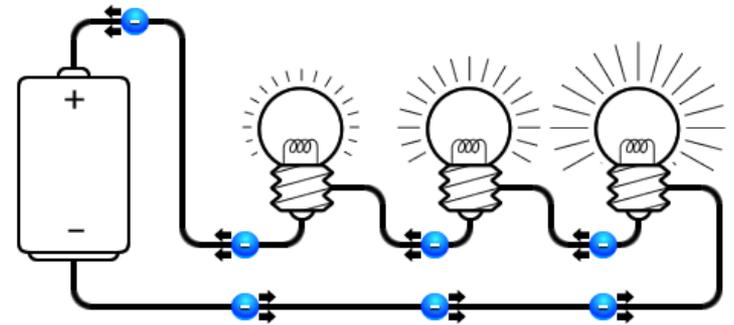- A single pathway through all parts of the circuit
- voltages add together,
- current stays constant.




Series Circuit

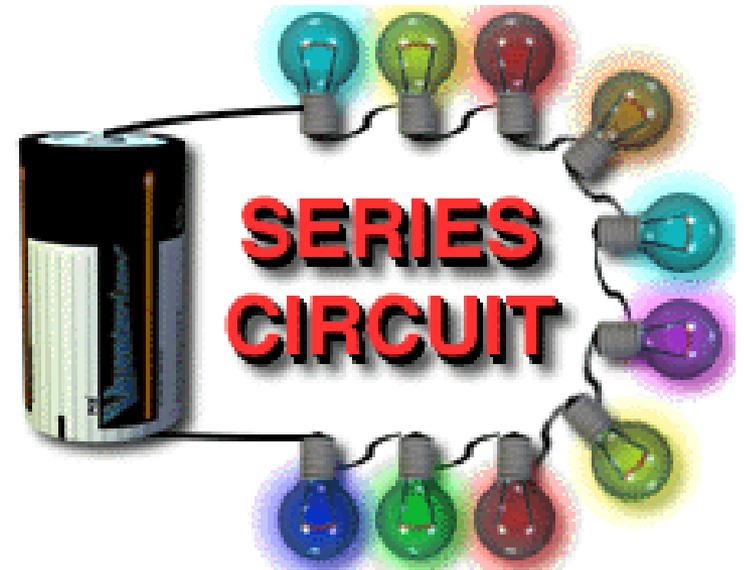
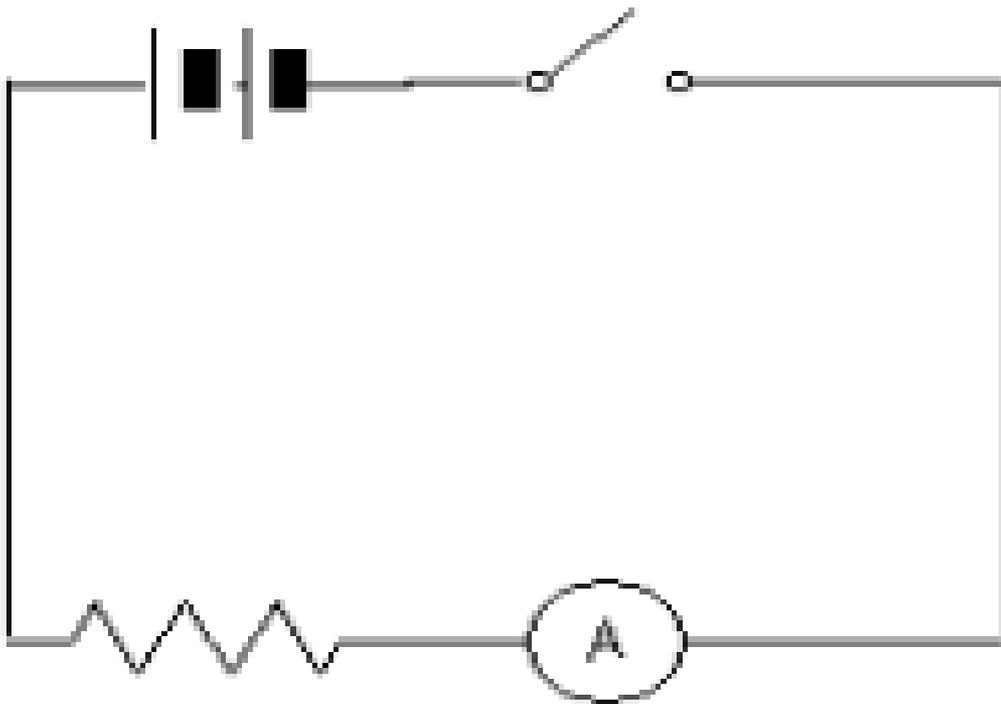






PARALLEL CIRCUIT

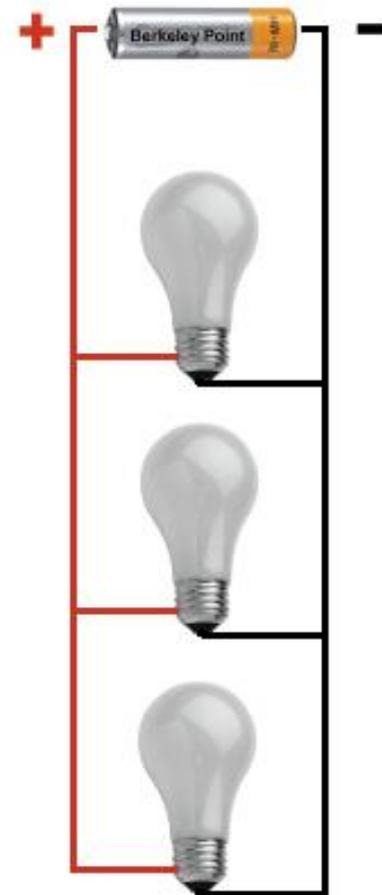- A branched pathway - more than one path for electrons
- voltage stays constant,
- currents add together.



Parallel Circuit

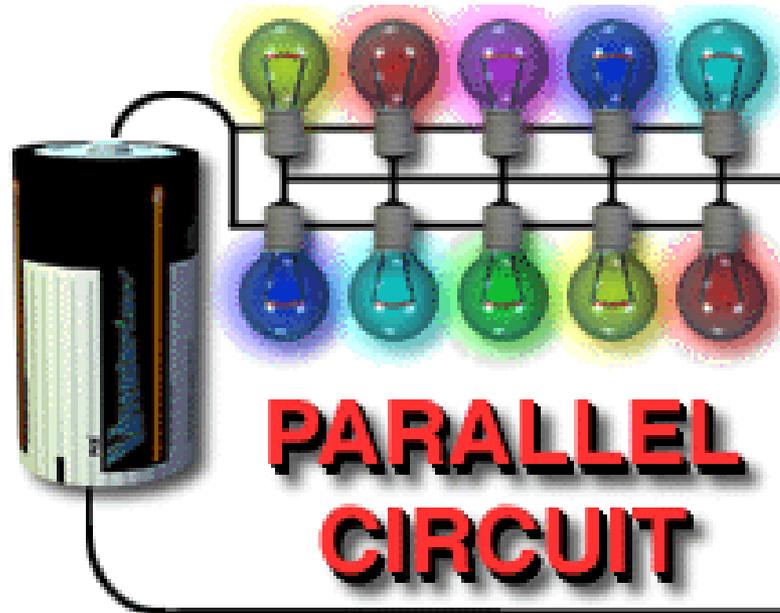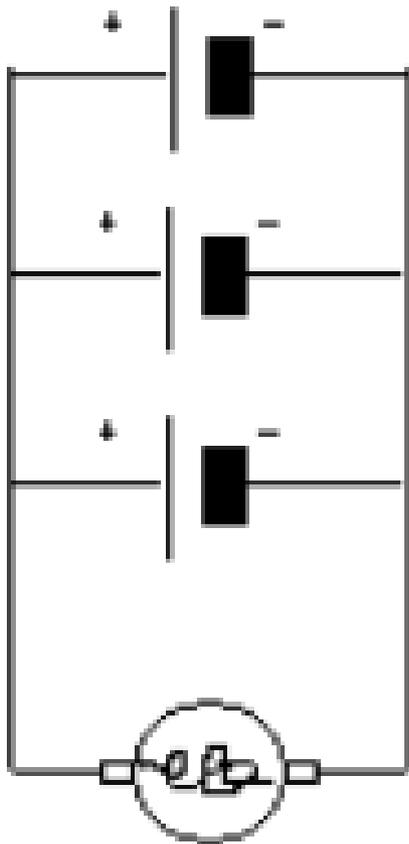

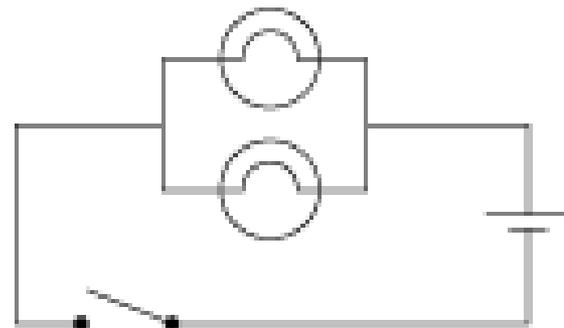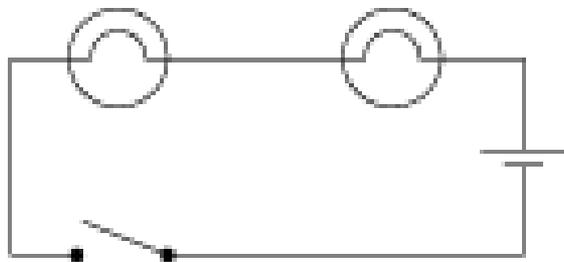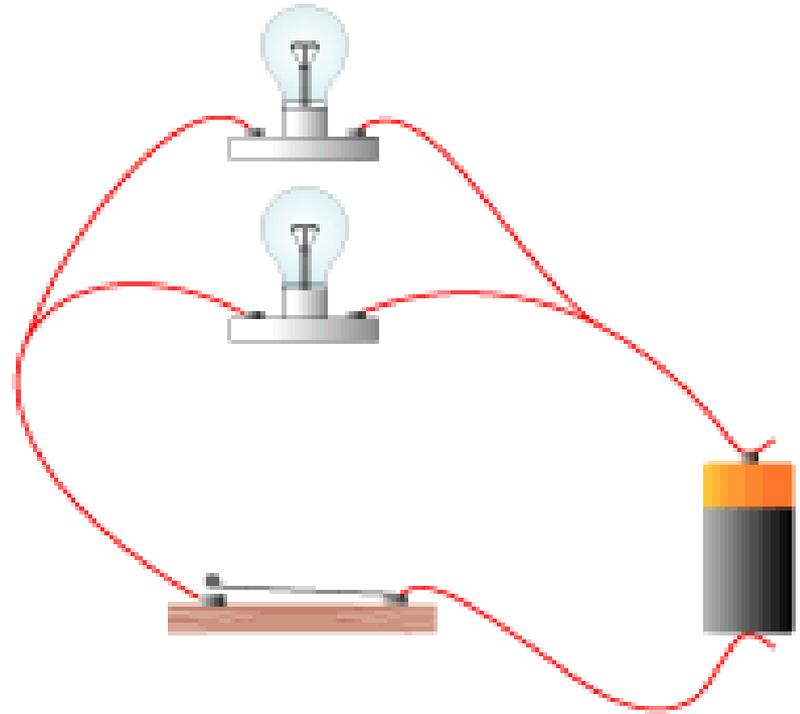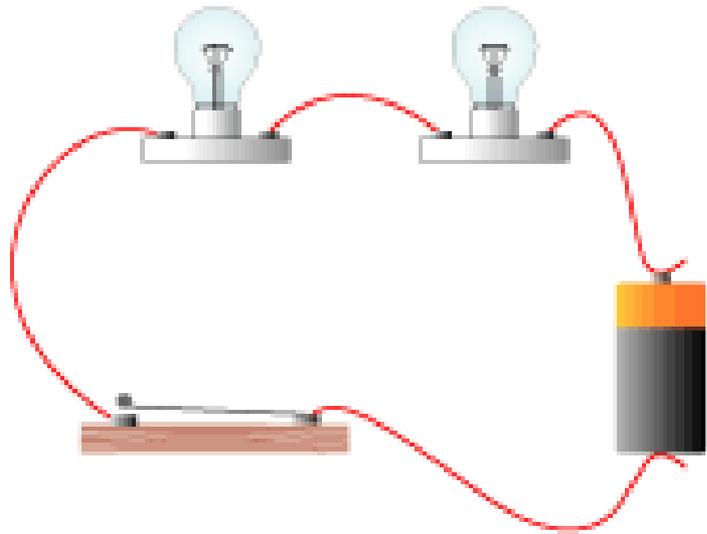

Continue lesson next day
Complete booklet 8.2

Current, Voltage, Resistance

- Current
 - a measure of the flow of electrons
 - measures in Amperes (A)
- Voltage
 - a measure of the potential energy per charge
 - measures in Volts (V)
- Resistance
 - a measure of the opposition to electron flow
 - measured in Ohms (Ω)

Units of Measure

- Charge
 - Measure in Coulombs (C)
 - Charge of one electron = 1.602×10^{-19} Coulombs
- Current
 - 1 Ampere = 1 Coulomb/second
- Voltage
 - 1 Volt = 1 Joule/Coulomb
- Resistance
 - 1 Ohm = 1 Volt/Ampere